

Types of data

Data storage

Circuits

Abstraction

Flip Flop

The basic unit of data is a **bit** — 0 or 1.

Bit string — 01101000


- chars
- numbers
- images
- sounds
- truth values
 - ◆ 0 – false
 - ◆ 1 – true

Data storage

Circuits

Abstraction

Flip Flop

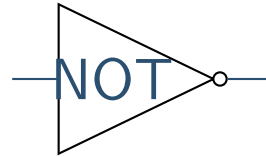

$$\neg 0 = 1; \quad \neg 1 = 0;$$

| x_1 | $\text{NOT}(x_1)$ |
|-------|-------------------|
| 0 | 1 |
| 1 | 0 |

Data storage

Circuits

Abstraction

Flip Flop



$$0 \wedge 0 = 0; 0 \wedge 1 = 0; 1 \wedge 0 = 0; 1 \wedge 1 = 1;$$

| x_1 | x_2 | $\text{AND}(x_1, x_2)$ |
|-------|-------|------------------------|
| 0 | 0 | 0 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

Data storage

Circuits

Abstraction

Flip Flop



$$0 \vee 0 = 0; 0 \vee 1 = 1; 1 \vee 0 = 1; 1 \vee 1 = 1;$$


| x_1 | x_2 | $\text{OR}(x_1, x_2)$ |
|-------|-------|-----------------------|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 1 |

Data storage

Circuits

Abstraction

Flip Flop

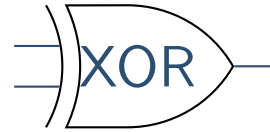

$$0 \oplus 0 = 0; 0 \oplus 1 = 1; 1 \oplus 0 = 1; 1 \oplus 1 = 0;$$

| x_1 | x_2 | $\text{XOR}(x_1, x_2)$ |
|-------|-------|------------------------|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

Data storage

Circuits

Abstraction

Flip Flop



$0 \text{ nand } 0 = 1$; $0 \text{ nand } 1 = 1$; $1 \text{ nand } 0 = 1$; $1 \text{ nand } 1 = 0$;

| x_1 | x_2 | $\text{NAND}(x_1, x_2)$ |
|-------|-------|-------------------------|
| 0 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |


Example circuit

Data storage

Circuits

Abstraction

Flip Flop

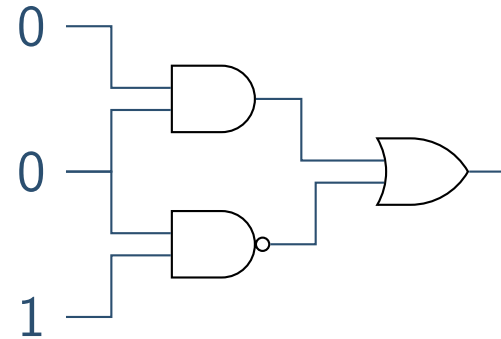

What are the top, bottom and rightmost gates?

- A. AND, NAND, XOR
- B. OR, NAND, XOR
- C. AND, NAND, OR
- D. OR, NAND, OR

Vote at m.socrative.com. Room number 415439.


Example circuit

Data storage

Circuits

Abstraction

Flip Flop

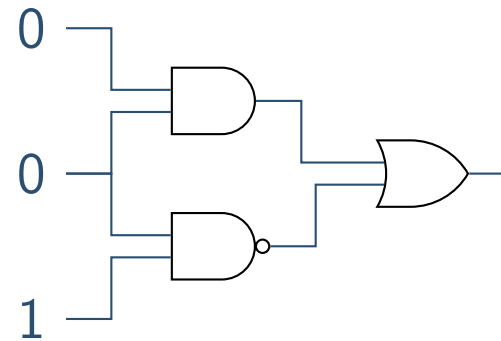

What are the top, bottom and rightmost gates?

C. AND, NAND, OR


Example circuit

Data storage

Circuits

Abstraction

Flip Flop

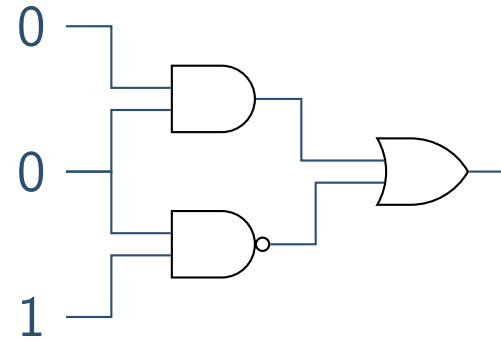

What is the output of this circuit?

- A. 0
- B. 1
- C. not defined

Vote at m.socrative.com. Room number 415439.


Example circuit

Data storage

Circuits

Abstraction


Flip Flop

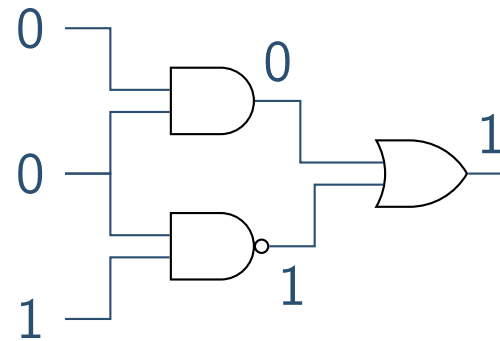

What is the output of this circuit?

B. 1

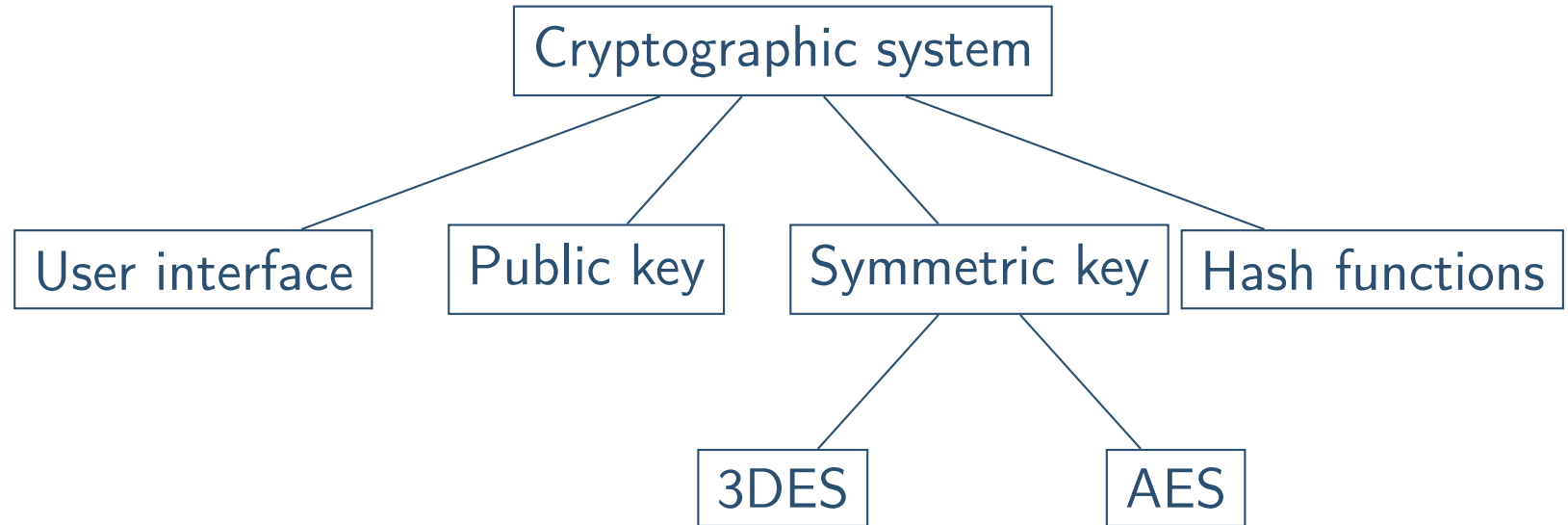Example: Top-down design - cryptographic system



Abstraction

Data storage

Circuits

Abstraction


Flip Flop

Things at higher levels need not know how things at lower levels function, only how to use them.

Interface, modularity, and modelling give:

- Structure — divide up work
- Independence between modules
(can re-implement without changing the rest)
- Ability to analyze
- Increased innovation, productivity
(don't need to re-invent the wheel)

Flip flop

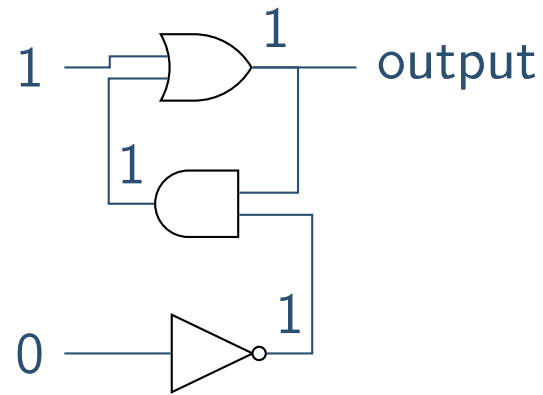


Note that this is stable.

Keeps same output until temporary outside pulse.


Can store a bit.

Flip flop

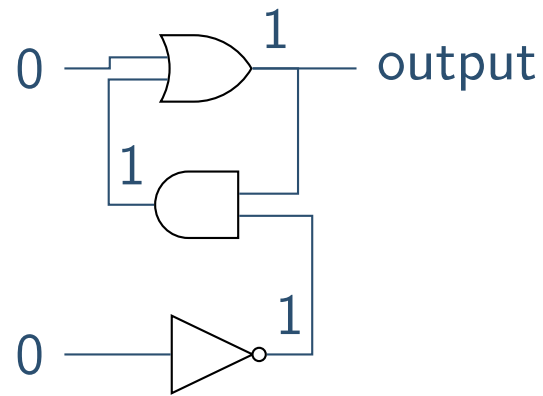


Note that this is stable.

Flip flop

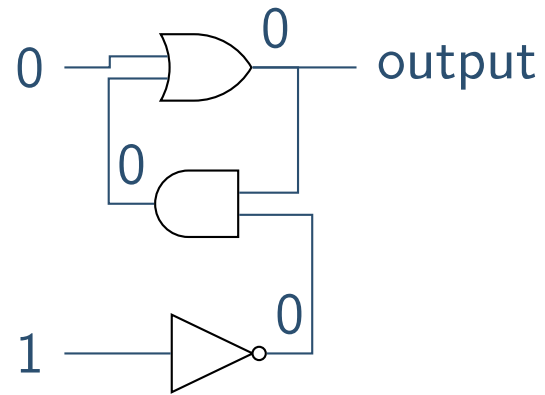

Note that this is stable.

Flip flop

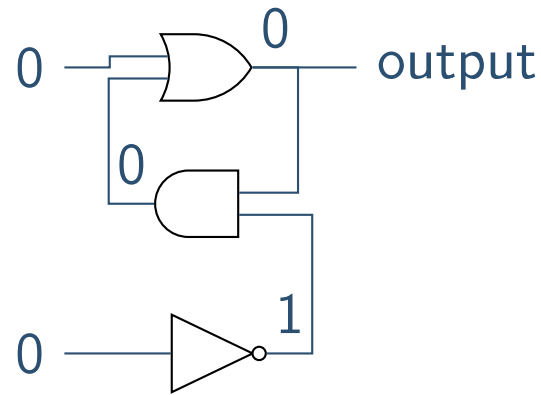

Note that this is stable.

But two different stable outputs are possible with input (0,0).

Flip flops can be implemented differently. Fig. 1.5, p. 38.

Abstraction: know input/output effect —
don't care about implementation.